


2.3.1: Series and Parallel Resistors and Equivalent Resistance (20 points total)

- Expected power dissipated by 1K Ω resistor (pre-lab analysis). (5 pts)

Expected Power: 1.45E-2 Watts

- Provide a schematic of the circuit below, including measured resistance values.

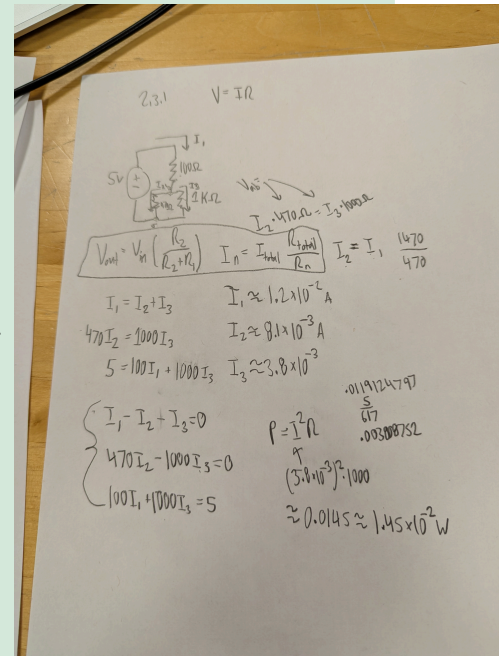100 Ω , 470 Ω , 1K Ω , schematic on the right



- Measured power dissipated by 1K Ω resistor (provide all measurements taken: actual resistance values, voltages, currents, power calculation). Comment on the agreement between measured and expected power dissipation – calculating a percent difference is always good! (8 pts)

1.0123K Ω , 462.62 Ω , 98.74 Ω , Our measured power dissipated by 1K Ω resistor is 1.41E-2W and our expected value was 1.45E-2W.

$$\text{Percent difference} = (1.41 - 1.45) / (1.45) * 100 = -2.65\% \text{ error}$$

- DEMO:** Have a teaching assistant initial this sheet, indicating that they have observed your circuit's operation. (4 pts)

TA Initials: _____